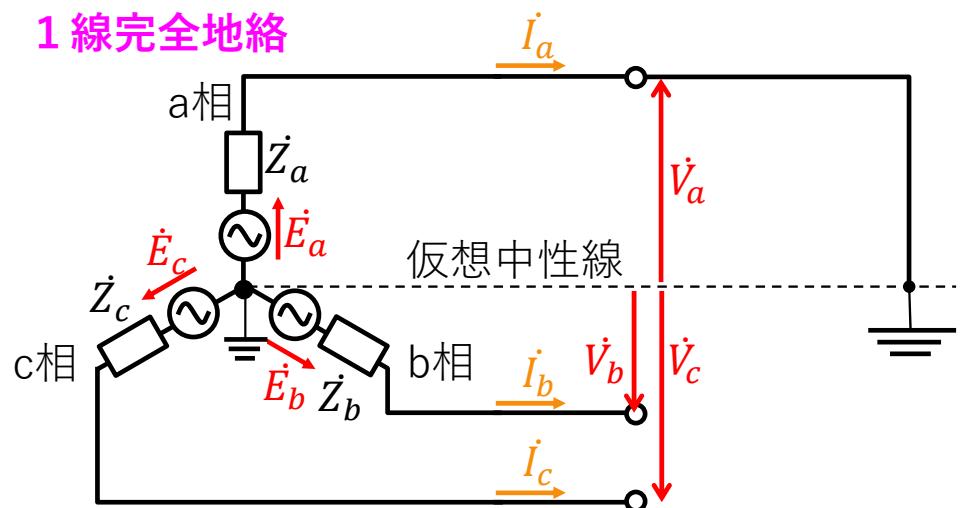


## 対称座標法（2）《無負荷発電機の地絡計算1》

### 1線完全地絡



回路条件

$$\dot{V}_a = 0 \cdots ①$$

$$\dot{I}_b = \dot{I}_c = 0 \cdots ②$$

$$②, ③, ④, ⑤, ⑥ \text{より } \dot{I}_0 = \dot{I}_1 = \dot{I}_2 \cdots ⑥$$

求める値

$$\dot{V}_b, \dot{V}_c, \dot{I}_a$$

発電機の基本式

$$\dot{V}_0 = -\dot{Z}_0 \dot{I}_0 \cdots ⑧$$

$$\dot{V}_1 = \dot{E}_a - \dot{Z}_1 \dot{I}_1 \cdots ⑨$$

$$\dot{V}_2 = -\dot{Z}_2 \dot{I}_2 \cdots ⑩$$

電流/電圧の定義式・対称分式

$$\dot{V}_a = \dot{V}_0 + \dot{V}_1 + \dot{V}_2 \cdots ⑦$$

$$\dot{V}_b = \dot{V}_0 + a^2 \dot{V}_1 + a \dot{V}_2 \cdots ⑬$$

$$\dot{V}_c = \dot{V}_0 + a \dot{V}_1 + a^2 \dot{V}_2 \cdots ⑭$$

$$\dot{V}_0 = \frac{1}{3} (\dot{V}_a + \dot{V}_b + \dot{V}_c)$$

$$\dot{V}_1 = \frac{1}{3} (\dot{V}_a + a \dot{V}_b + a^2 \dot{V}_c)$$

$$\dot{V}_2 = \frac{1}{3} (\dot{V}_a + a^2 \dot{V}_b + a \dot{V}_c)$$

$$\dot{I}_a = \dot{I}_0 + \dot{I}_1 + \dot{I}_2 \cdots ⑫$$

$$\dot{I}_b = \dot{I}_0 + a^2 \dot{I}_1 + a \dot{I}_2$$

$$\dot{I}_c = \dot{I}_0 + a \dot{I}_1 + a^2 \dot{I}_2$$

$$\dot{I}_0 = \frac{1}{3} (\dot{I}_a + \dot{I}_b + \dot{I}_c) \cdots ⑬$$

$$\dot{I}_1 = \frac{1}{3} (\dot{I}_a + a \dot{I}_b + a^2 \dot{I}_c) \cdots ⑭$$

$$\dot{I}_2 = \frac{1}{3} (\dot{I}_a + a^2 \dot{I}_b + a \dot{I}_c) \cdots ⑮$$

$$⑦ \text{に } ①, ⑥, ⑧, ⑨, ⑩ \text{を代入 } \dot{V}_a = -\dot{Z}_0 \dot{I}_0 + \dot{E}_a - \dot{Z}_1 \dot{I}_1 - \dot{Z}_2 \dot{I}_2 = \dot{E}_a - (\dot{Z}_0 + \dot{Z}_1 + \dot{Z}_2) \dot{I}_0 = 0$$

$$\dot{I}_0 = \frac{\dot{E}_a}{\dot{Z}_0 + \dot{Z}_1 + \dot{Z}_2} \cdots ⑪$$

$$⑫ \text{に } ⑥, ⑪ \text{を代入 } \dot{I}_a = \dot{I}_0 + \dot{I}_1 + \dot{I}_2 = 3\dot{I}_0 = \frac{3\dot{E}_a}{\dot{Z}_0 + \dot{Z}_1 + \dot{Z}_2}$$

$$⑬ \text{に } ⑥, ⑧, ⑨, ⑩, ⑪ \text{を代入 } \dot{V}_b = \frac{(a^2 - 1)\dot{Z}_0 + (a^2 - a)\dot{Z}_2}{\dot{Z}_0 + \dot{Z}_1 + \dot{Z}_2} \dot{E}_a$$

$$⑭ \text{に } ⑥, ⑧, ⑨, ⑩, ⑪ \text{を代入 } \dot{V}_c = \frac{(a - 1)\dot{Z}_0 + (a - a^2)\dot{Z}_2}{\dot{Z}_0 + \dot{Z}_1 + \dot{Z}_2} \dot{E}_a$$

## 対称座標法 (2)

### 1線完全地絡の計算

$$\dot{V}_a = 0 \cdots ①$$

$$\dot{I}_b = \dot{I}_c = 0 \cdots ②$$

②,③,④,⑤より、

$$\left. \begin{array}{l} I_0 = \frac{1}{3}(I_a + I_b + I_c) = \frac{1}{3}\dot{I}_a \\ I_1 = \frac{1}{3}(I_a + a\dot{I}_b + a^2\dot{I}_c) = \frac{1}{3}\dot{I}_a \\ I_2 = \frac{1}{3}(I_a + a^2\dot{I}_b + a\dot{I}_c) = \frac{1}{3}\dot{I}_a \end{array} \right\} \dot{I}_0 = \dot{I}_1 = \dot{I}_2 \cdots ⑥$$

⑦に①,⑥,⑧,⑨,⑩を代入

$$\begin{aligned} \dot{V}_a &= \dot{V}_0 + \dot{V}_1 + \dot{V}_2 = -\dot{Z}_0\dot{I}_0 + \dot{E}_a - \dot{Z}_1\dot{I}_1 - \dot{Z}_2\dot{I}_2 \\ &= \dot{E}_a - (\dot{Z}_0 + \dot{Z}_1 + \dot{Z}_2)\dot{I}_0 = 0 \end{aligned}$$

$$\dot{I}_0 = \frac{\dot{E}_a}{\dot{Z}_0 + \dot{Z}_1 + \dot{Z}_2} \cdots ⑪$$

⑫に⑥,⑪を代入

$$\dot{I}_a = \dot{I}_0 + \dot{I}_1 + \dot{I}_2 = 3\dot{I}_0 = \frac{3\dot{E}_a}{\dot{Z}_0 + \dot{Z}_1 + \dot{Z}_2}$$

⑬に,⑥,⑧,⑨,⑩,⑪を代入

$$\begin{aligned} \dot{V}_b &= \dot{V}_0 + a^2\dot{V}_1 + a\dot{V}_2 \\ &= -\dot{Z}_0\dot{I}_0 + a^2(\dot{E}_a - \dot{Z}_1\dot{I}_0) - a\dot{Z}_2\dot{I}_0 \\ &= a^2\dot{E}_a - (\dot{Z}_0 + a^2\dot{Z}_1 + a\dot{Z}_2)\dot{I}_0 \\ &= \frac{a^2(\dot{Z}_0 + \dot{Z}_1 + \dot{Z}_2)}{\dot{Z}_0 + \dot{Z}_1 + \dot{Z}_2} \dot{E}_a - \frac{(\dot{Z}_0 + a^2\dot{Z}_1 + a\dot{Z}_2)}{\dot{Z}_0 + \dot{Z}_1 + \dot{Z}_2} \dot{E}_a \\ &= \frac{(a^2 - 1)\dot{Z}_0 + (a^2 - a)\dot{Z}_2}{\dot{Z}_0 + \dot{Z}_1 + \dot{Z}_2} \dot{E}_a \end{aligned}$$

⑭に,⑥,⑧,⑨,⑩,⑪を代入

$$\begin{aligned} \dot{V}_c &= \dot{V}_0 + a\dot{V}_1 + a^2\dot{V}_2 \\ &= -\dot{Z}_0\dot{I}_0 + a(\dot{E}_a - \dot{Z}_1\dot{I}_0) - a^2\dot{Z}_2\dot{I}_0 \\ &= a\dot{E}_a - (\dot{Z}_0 + a\dot{Z}_1 + a^2\dot{Z}_2)\dot{I}_0 \\ &= \frac{a(\dot{Z}_0 + \dot{Z}_1 + \dot{Z}_2)}{\dot{Z}_0 + \dot{Z}_1 + \dot{Z}_2} \dot{E}_a - \frac{(\dot{Z}_0 + a\dot{Z}_1 + a^2\dot{Z}_2)}{\dot{Z}_0 + \dot{Z}_1 + \dot{Z}_2} \dot{E}_a \\ &= \frac{(a - 1)\dot{Z}_0 + (a - a^2)\dot{Z}_2}{\dot{Z}_0 + \dot{Z}_1 + \dot{Z}_2} \dot{E}_a \end{aligned}$$

### 発電機の基本式

$$\dot{V}_0 = -\dot{Z}_0\dot{I}_0 \cdots ⑧$$

$$\dot{V}_1 = \dot{E}_a - \dot{Z}_1\dot{I}_1 \cdots ⑨$$

$$\dot{V}_2 = -\dot{Z}_2\dot{I}_2 \cdots ⑩$$

### 電流/電圧の定義式・対称分式

$$\dot{V}_a = \dot{V}_0 + \dot{V}_1 + \dot{V}_2 \cdots ⑦$$

$$\dot{V}_b = \dot{V}_0 + a^2\dot{V}_1 + a\dot{V}_2 \cdots ⑬$$

$$\dot{V}_c = \dot{V}_0 + a\dot{V}_1 + a^2\dot{V}_2 \cdots ⑭$$

$$\dot{V}_0 = \frac{1}{3}(\dot{V}_a + \dot{V}_b + \dot{V}_c)$$

$$\dot{V}_1 = \frac{1}{3}(\dot{V}_a + a\dot{V}_b + a^2\dot{V}_c)$$

$$\dot{V}_2 = \frac{1}{3}(\dot{V}_a + a^2\dot{V}_b + a\dot{V}_c)$$

$$\dot{I}_a = \dot{I}_0 + \dot{I}_1 + \dot{I}_2 \cdots ⑫$$

$$\dot{I}_b = \dot{I}_0 + a^2\dot{I}_1 + a\dot{I}_2$$

$$\dot{I}_c = \dot{I}_0 + a\dot{I}_1 + a^2\dot{I}_2$$


$$\dot{I}_0 = \frac{1}{3}(\dot{I}_a + \dot{I}_b + \dot{I}_c) \cdots ③$$

$$\dot{I}_1 = \frac{1}{3}(\dot{I}_a + a\dot{I}_b + a^2\dot{I}_c) \cdots ④$$

$$\dot{I}_2 = \frac{1}{3}(\dot{I}_a + a^2\dot{I}_b + a\dot{I}_c) \cdots ⑤$$

## 対称座標法（2）《無負荷発電機の地絡計算2》

### 1線不完全地絡

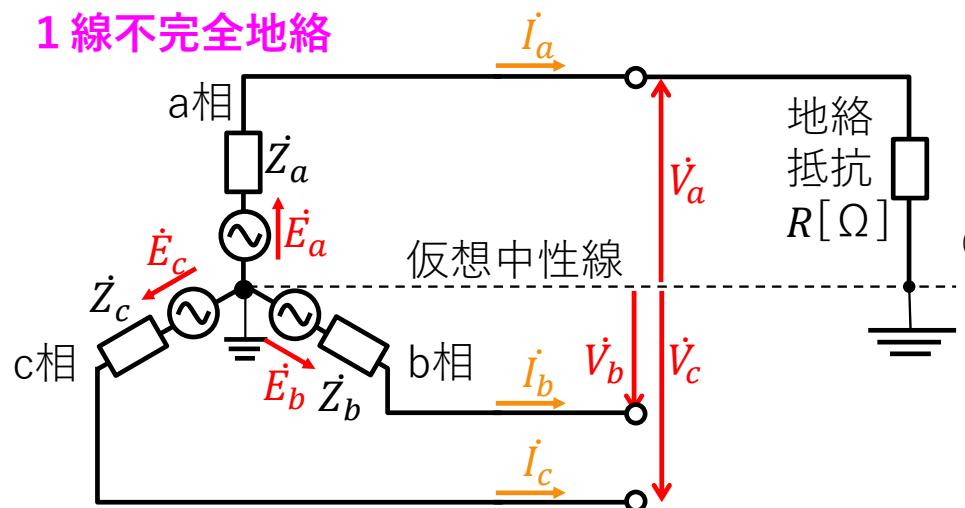

### 回路条件

$$\dot{V}_a = RI_a \quad \dots \textcircled{1}$$

$$\dot{I}_b = \dot{I}_c = 0 \quad \dots \textcircled{2}$$

$$\textcircled{2}, \textcircled{3}, \textcircled{4}, \textcircled{5} \text{より}, \dot{I}_0 = \dot{I}_1 = \dot{I}_2 \quad \dots \textcircled{6}$$

### 発電機の基本式

$$\dot{V}_0 = -\dot{Z}_0 \dot{I}_0 \quad \dots \textcircled{8}$$

$$\dot{V}_1 = \dot{E}_a - \dot{Z}_1 \dot{I}_1 \quad \dots \textcircled{9}$$

$$\dot{V}_2 = -\dot{Z}_2 \dot{I}_2 \quad \dots \textcircled{10}$$

### 電流/電圧の定義式・対称分式

$$\dot{V}_a = \dot{V}_0 + \dot{V}_1 + \dot{V}_2 \quad \dots \textcircled{7}$$

$$\dot{V}_b = \dot{V}_0 + a^2 \dot{V}_1 + a \dot{V}_2 \quad \dots \textcircled{13}$$

$$\dot{V}_c = \dot{V}_0 + a \dot{V}_1 + a^2 \dot{V}_2 \quad \dots \textcircled{14}$$

$$\dot{V}_0 = \frac{1}{3} (\dot{V}_a + \dot{V}_b + \dot{V}_c)$$

$$\dot{V}_1 = \frac{1}{3} (\dot{V}_a + a \dot{V}_b + a^2 \dot{V}_c)$$

$$\dot{V}_2 = \frac{1}{3} (\dot{V}_a + a^2 \dot{V}_b + a \dot{V}_c)$$

$$\dot{I}_a = \dot{I}_0 + \dot{I}_1 + \dot{I}_2 \quad \dots \textcircled{12}$$

$$\dot{I}_b = \dot{I}_0 + a^2 \dot{I}_1 + a \dot{I}_2$$

$$\dot{I}_c = \dot{I}_0 + a \dot{I}_1 + a^2 \dot{I}_2$$

$$\dot{I}_0 = \frac{1}{3} (\dot{I}_a + \dot{I}_b + \dot{I}_c) \quad \dots \textcircled{3}$$

$$\dot{I}_1 = \frac{1}{3} (\dot{I}_a + a \dot{I}_b + a^2 \dot{I}_c) \quad \dots \textcircled{4}$$

$$\dot{I}_2 = \frac{1}{3} (\dot{I}_a + a^2 \dot{I}_b + a \dot{I}_c) \quad \dots \textcircled{5}$$

$$\textcircled{7} \text{に} \textcircled{1}, \textcircled{6}, \textcircled{8}, \textcircled{9}, \textcircled{10} \text{を代入 } \dot{V}_a = -\dot{Z}_0 \dot{I}_0 + \dot{E}_a - \dot{Z}_1 \dot{I}_1 - \dot{Z}_2 \dot{I}_2 = \dot{E}_a - (\dot{Z}_0 + \dot{Z}_1 + \dot{Z}_2) \dot{I}_0 = 3R \dot{I}_0$$

$$\dot{I}_0 = \frac{\dot{E}_a}{\dot{Z}_0 + \dot{Z}_1 + \dot{Z}_2 + 3R} \quad \dots \textcircled{11}$$

$$\textcircled{12} \text{に} \textcircled{6}, \textcircled{11} \text{を代入 } \dot{I}_a = \dot{I}_0 + \dot{I}_1 + \dot{I}_2 = 3\dot{I}_0 = \frac{3\dot{E}_a}{\dot{Z}_0 + \dot{Z}_1 + \dot{Z}_2 + 3R}$$

$$\textcircled{13} \text{に} \textcircled{6}, \textcircled{8}, \textcircled{9}, \textcircled{10}, \textcircled{11} \text{を代入 } \dot{V}_b = \frac{(a^2 - 1)\dot{Z}_0 + (a^2 - a)\dot{Z}_2 + 3a^2 R}{\dot{Z}_0 + \dot{Z}_1 + \dot{Z}_2 + 3R} \dot{E}_a$$

$$\textcircled{14} \text{に} \textcircled{6}, \textcircled{8}, \textcircled{9}, \textcircled{10}, \textcircled{11} \text{を代入 } \dot{V}_c = \frac{(a - 1)\dot{Z}_0 + (a - a^2)\dot{Z}_2 + 3a R}{\dot{Z}_0 + \dot{Z}_1 + \dot{Z}_2 + 3R} \dot{E}_a$$

## 対称座標法 (2)

### 1線不完全地絡の計算

$$\dot{V}_a = RI_a \cdots ①$$

$$\dot{I}_b = \dot{I}_c = 0 \cdots ②$$

②,③,④,⑤より、

$$\left. \begin{array}{l} I_0 = \frac{1}{3}(I_a + I_b + I_c) = \frac{1}{3}I_a \\ I_1 = \frac{1}{3}(I_a + aI_b + a^2I_c) = \frac{1}{3}I_a \\ I_2 = \frac{1}{3}(I_a + a^2I_b + aI_c) = \frac{1}{3}I_a \end{array} \right\} \quad I_0 = I_1 = I_2 \cdots ⑥$$

⑦に①,⑥,⑧,⑨,⑩を代入

$$\begin{aligned} \dot{V}_a &= \dot{V}_0 + \dot{V}_1 + \dot{V}_2 = -\dot{Z}_0\dot{I}_0 + \dot{E}_a - \dot{Z}_1\dot{I}_1 - \dot{Z}_2\dot{I}_2 \\ &= \dot{E}_a - (\dot{Z}_0 + \dot{Z}_1 + \dot{Z}_2)\dot{I}_0 = RI_a = 3RI_0 \\ &\quad RI_a = R(\dot{I}_0 + \dot{I}_1 + \dot{I}_2) = 3RI_a \end{aligned}$$

$$I_0 = \frac{\dot{E}_a}{\dot{Z}_0 + \dot{Z}_1 + \dot{Z}_2 + 3R} \cdots ⑪$$

⑫に⑥,⑪を代入

$$\dot{I}_a = \dot{I}_0 + \dot{I}_1 + \dot{I}_2 = 3\dot{I}_0 = \frac{3\dot{E}_a}{\dot{Z}_0 + \dot{Z}_1 + \dot{Z}_2 + 3R}$$

⑬に,⑥,⑧,⑨,⑩,⑪を代入

$$\begin{aligned} \dot{V}_b &= \dot{V}_0 + a^2\dot{V}_1 + a\dot{V}_2 \\ &= -\dot{Z}_0\dot{I}_0 + a^2(\dot{E}_a - \dot{Z}_1\dot{I}_0) - a\dot{Z}_2\dot{I}_0 \\ &= a^2\dot{E}_a - (\dot{Z}_0 + a^2\dot{Z}_1 + a\dot{Z}_2)\dot{I}_0 \\ &= \frac{a^2(\dot{Z}_0 + \dot{Z}_1 + \dot{Z}_2 + 3R)}{\dot{Z}_0 + \dot{Z}_1 + \dot{Z}_2 + 3R}\dot{E}_a - \frac{(\dot{Z}_0 + a^2\dot{Z}_1 + a\dot{Z}_2)}{\dot{Z}_0 + \dot{Z}_1 + \dot{Z}_2 + 3R}\dot{E}_a \\ &= \frac{(a^2 - 1)\dot{Z}_0 + (a^2 - a)\dot{Z}_2 + 3a^2R}{\dot{Z}_0 + \dot{Z}_1 + \dot{Z}_2 + 3R}\dot{E}_a \end{aligned}$$

⑭に,⑥,⑧,⑨,⑩,⑪を代入

$$\begin{aligned} \dot{V}_c &= \dot{V}_0 + a\dot{V}_1 + a^2\dot{V}_2 \\ &= -\dot{Z}_0\dot{I}_0 + a(\dot{E}_a - \dot{Z}_1\dot{I}_0) - a^2\dot{Z}_2\dot{I}_0 \\ &= a\dot{E}_a - (\dot{Z}_0 + a\dot{Z}_1 + a^2\dot{Z}_2)\dot{I}_0 \\ &= \frac{a(\dot{Z}_0 + \dot{Z}_1 + \dot{Z}_2 + 3R)}{\dot{Z}_0 + \dot{Z}_1 + \dot{Z}_2 + 3R}\dot{E}_a - \frac{(\dot{Z}_0 + a\dot{Z}_1 + a^2\dot{Z}_2)}{\dot{Z}_0 + \dot{Z}_1 + \dot{Z}_2 + 3R}\dot{E}_a \\ &= \frac{(a - 1)\dot{Z}_0 + (a - a^2)\dot{Z}_2 + 3aR}{\dot{Z}_0 + \dot{Z}_1 + \dot{Z}_2 + 3R}\dot{E}_a \end{aligned}$$

### 発電機の基本式

$$\dot{V}_0 = -\dot{Z}_0\dot{I}_0 \cdots ⑧$$

$$\dot{V}_1 = \dot{E}_a - \dot{Z}_1\dot{I}_1 \cdots ⑨$$

$$\dot{V}_2 = -\dot{Z}_2\dot{I}_2 \cdots ⑩$$

### 電流/電圧の定義式・対称分式

$$\dot{V}_a = \dot{V}_0 + \dot{V}_1 + \dot{V}_2 \cdots ⑦$$

$$\dot{V}_b = \dot{V}_0 + a^2\dot{V}_1 + a\dot{V}_2 \cdots ⑬$$

$$\dot{V}_c = \dot{V}_0 + a\dot{V}_1 + a^2\dot{V}_2 \cdots ⑭$$

$$\dot{V}_0 = \frac{1}{3}(\dot{V}_a + \dot{V}_b + \dot{V}_c)$$

$$\dot{V}_1 = \frac{1}{3}(\dot{V}_a + a\dot{V}_b + a^2\dot{V}_c)$$

$$\dot{V}_2 = \frac{1}{3}(\dot{V}_a + a^2\dot{V}_b + a\dot{V}_c)$$

$$\dot{I}_a = \dot{I}_0 + \dot{I}_1 + \dot{I}_2 \cdots ⑫$$

$$\dot{I}_b = \dot{I}_0 + a^2\dot{I}_1 + a\dot{I}_2$$

$$\dot{I}_c = \dot{I}_0 + a\dot{I}_1 + a^2\dot{I}_2$$


$$\dot{I}_0 = \frac{1}{3}(\dot{I}_a + \dot{I}_b + \dot{I}_c) \cdots ③$$

$$\dot{I}_1 = \frac{1}{3}(\dot{I}_a + a\dot{I}_b + a^2\dot{I}_c) \cdots ④$$

$$\dot{I}_2 = \frac{1}{3}(\dot{I}_a + a^2\dot{I}_b + a\dot{I}_c) \cdots ⑤$$

## 対称座標法（2）《無負荷発電機の地絡計算3》

### 2線完全地絡

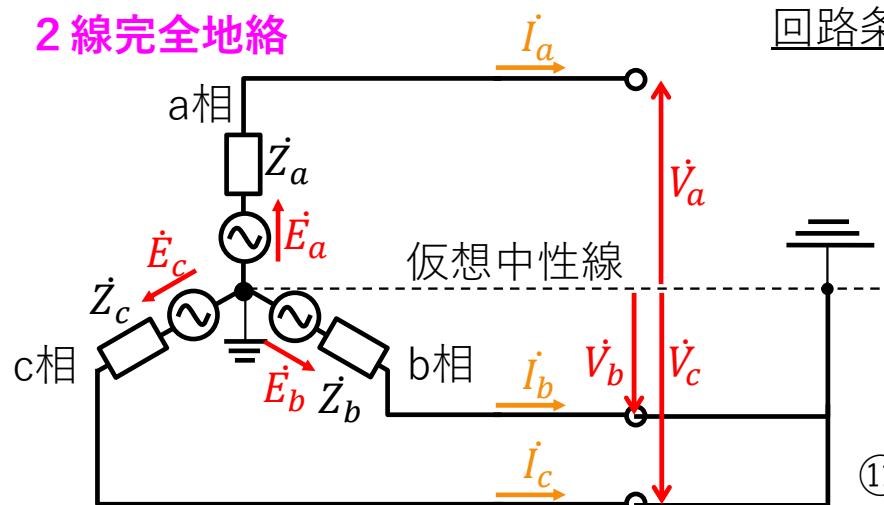

回路条件  $\dot{V}_b = \dot{V}_c = 0 \cdots ①$   $\dot{I}_a = 0 \cdots ②$

$$①, ③, ④ \text{より}, \dot{V}_0 = \dot{V}_1 = \dot{V}_2 \cdots ⑤$$

⑥に②, ⑤, ⑦, ⑧, ⑨を代入

$$\dot{I}_a = \dot{I}_0 + \dot{I}_1 + \dot{I}_2 = -\frac{\dot{V}_0}{Z_0} + \frac{\dot{E}_a - \dot{V}_0}{Z_1} - \frac{\dot{V}_0}{Z_2} = 0$$

$$\dot{V}_0 = \frac{Z_0 Z_2}{Z_0 Z_1 + Z_1 Z_2 + Z_0 Z_2} \dot{E}_a = \dot{V}_1 = \dot{V}_2 \cdots ⑩$$

$$⑪ \text{に} ⑩ \text{を代入 } \dot{V}_a = \frac{3 Z_0 Z_2}{Z_0 Z_1 + Z_1 Z_2 + Z_0 Z_2} \dot{E}_a$$

⑦, ⑩より

$$\dot{I}_0 = -\frac{Z_2}{Z_0 Z_1 + Z_1 Z_2 + Z_0 Z_2} \dot{E}_a \cdots ⑫$$

⑧, ⑩より

$$\dot{I}_1 = \frac{Z_0 + Z_2}{Z_0 Z_1 + Z_1 Z_2 + Z_0 Z_2} \dot{E}_a \cdots ⑬$$

⑨, ⑩より

$$\dot{I}_2 = -\frac{Z_0}{Z_0 Z_1 + Z_1 Z_2 + Z_0 Z_2} \dot{E}_a \cdots ⑭$$

⑮に⑫, ⑬, ⑭を代入

$$\dot{I}_b = \frac{(a^2 - a) Z_0 + (a^2 - 1) Z_2}{Z_0 Z_1 + Z_1 Z_2 + Z_0 Z_2} \dot{E}_a$$

⑯に⑫, ⑬, ⑭を代入

$$\dot{I}_c = \frac{(a - a^2) Z_0 + (a - 1) Z_2}{Z_0 Z_1 + Z_1 Z_2 + Z_0 Z_2} \dot{E}_a$$

なお、 $\dot{I}_b + \dot{I}_c = 3\dot{I}_0$ となる

### 発電機の基本式

$$\dot{V}_0 = -Z_0 \dot{I}_0 \cdots ⑦$$

$$\dot{V}_1 = \dot{E}_a - Z_1 \dot{I}_1 \cdots ⑧$$

$$\dot{V}_2 = -Z_2 \dot{I}_2 \cdots ⑨$$

### 電流/電圧の定義式・対称分式

$$\dot{V}_a = \dot{V}_0 + \dot{V}_1 + \dot{V}_2 \cdots ⑪$$

$$\dot{V}_b = \dot{V}_0 + a^2 \dot{V}_1 + a \dot{V}_2 \cdots ⑬$$

$$\dot{V}_c = \dot{V}_0 + a \dot{V}_1 + a^2 \dot{V}_2 \cdots ⑭$$

$$\dot{V}_0 = \frac{1}{3} (\dot{V}_a + \dot{V}_b + \dot{V}_c)$$

$$\dot{V}_1 = \frac{1}{3} (\dot{V}_a + a \dot{V}_b + a^2 \dot{V}_c)$$

$$\dot{V}_2 = \frac{1}{3} (\dot{V}_a + a^2 \dot{V}_b + a \dot{V}_c)$$

$$\dot{I}_a = \dot{I}_0 + \dot{I}_1 + \dot{I}_2 \cdots ⑥$$

$$\dot{I}_b = \dot{I}_0 + a^2 \dot{I}_1 + a \dot{I}_2 \cdots ⑮$$

$$\dot{I}_c = \dot{I}_0 + a \dot{I}_1 + a^2 \dot{I}_2 \cdots ⑯$$

$$\dot{I}_0 = \frac{1}{3} (\dot{I}_a + \dot{I}_b + \dot{I}_c)$$

$$\dot{I}_1 = \frac{1}{3} (\dot{I}_a + a \dot{I}_b + a^2 \dot{I}_c)$$

$$\dot{I}_2 = \frac{1}{3} (\dot{I}_a + a^2 \dot{I}_b + a \dot{I}_c)$$

## 対称座標法 (2)

## 2線完全地絡の計算

$$\dot{V}_b = \dot{V}_c = 0 \quad \dots \textcircled{1} \quad \dot{I}_a = 0 \quad \dots \textcircled{2}$$

①より  $\dot{V}_b - \dot{V}_c = 0$  に, ③, ④を代入

$$\dot{V}_0 + a^2\dot{V}_1 + a\dot{V}_2 - (\dot{V}_0 + a\dot{V}_1 + a^2\dot{V}_2) = 0$$

$$(a^2 - a)(\dot{V}_1 - \dot{V}_2) = 0$$

$$a^2 - a \neq 0 \text{ より } \dot{V}_1 = \dot{V}_2$$

$$\textcircled{3} \text{ より } \dot{V}_b = \dot{V}_0 + (a^2 + a)\dot{V}_1 = 0$$

$$a^2 + a = -1 \text{ より } \dot{V}_0 = \dot{V}_1 = \dot{V}_2 \quad \dots \textcircled{5}$$

⑥に②, ⑦, ⑧, ⑨を代入

$$\dot{I}_a = \dot{I}_0 + \dot{I}_1 + \dot{I}_2 = -\frac{\dot{V}_0}{Z_0} + \frac{E_a - \dot{V}_0}{Z_1} - \frac{\dot{V}_0}{Z_2} = 0$$

$$\frac{E_a}{Z_1} - \left( \frac{1}{Z_0} + \frac{1}{Z_1} + \frac{1}{Z_2} \right) \dot{V}_0 = 0$$

$$\dot{V}_0 = \frac{Z_0 Z_2}{Z_0 Z_1 + Z_1 Z_2 + Z_0 Z_2} E_a = \dot{V}_1 = \dot{V}_2 \quad \dots \textcircled{10}$$

$$\begin{aligned} \textcircled{11} \text{ に } \textcircled{10} \text{ を代入 } \quad \dot{V}_a &= \dot{V}_0 + \dot{V}_1 + \dot{V}_2 = 3\dot{V}_0 \\ &= \frac{3Z_0 Z_2}{Z_0 Z_1 + Z_1 Z_2 + Z_0 Z_2} E_a \end{aligned}$$

$$\textcircled{7}, \textcircled{10} \text{ より } \dot{I}_0 = -\frac{\dot{V}_0}{Z_0} = -\frac{\dot{Z}_2}{Z_0 Z_1 + Z_1 Z_2 + Z_0 Z_2} E_a \quad \dots \textcircled{12}$$

$$\textcircled{8}, \textcircled{10} \text{ より } \dot{I}_1 = \frac{E_a - \dot{V}_0}{Z_1} = \frac{\dot{Z}_0 + \dot{Z}_2}{Z_0 Z_1 + Z_1 Z_2 + Z_0 Z_2} E_a \quad \dots \textcircled{13}$$

$$\textcircled{9}, \textcircled{10} \text{ より } \dot{I}_2 = -\frac{\dot{V}_0}{Z_2} = -\frac{\dot{Z}_0}{Z_0 Z_1 + Z_1 Z_2 + Z_0 Z_2} E_a \quad \dots \textcircled{14}$$

⑮に⑫, ⑬, ⑭を代入

$$\begin{aligned} \dot{I}_b &= \dot{I}_0 + a^2 \dot{I}_1 + a \dot{I}_2 = \frac{-\dot{Z}_2 + a^2(\dot{Z}_0 + \dot{Z}_2) - a \dot{Z}_0}{Z_0 Z_1 + Z_1 Z_2 + Z_0 Z_2} E_a \\ &= \frac{(a^2 - a) \dot{Z}_0 + (a^2 - 1) \dot{Z}_2}{Z_0 Z_1 + Z_1 Z_2 + Z_0 Z_2} E_a \end{aligned}$$

⑯に⑫, ⑬, ⑭を代入

$$\begin{aligned} \dot{I}_c &= \dot{I}_0 + a \dot{I}_1 + a^2 \dot{I}_2 = \frac{-\dot{Z}_2 + a(\dot{Z}_0 + \dot{Z}_2) - a^2 \dot{Z}_0}{Z_0 Z_1 + Z_1 Z_2 + Z_0 Z_2} E_a \\ &= \frac{(a - a^2) \dot{Z}_0 + (a - 1) \dot{Z}_2}{Z_0 Z_1 + Z_1 Z_2 + Z_0 Z_2} E_a \end{aligned}$$

$$\text{なお、 } \dot{I}_b + \dot{I}_c = \frac{-3\dot{Z}_2}{Z_0 Z_1 + Z_1 Z_2 + Z_0 Z_2} E_a = 3\dot{I}_0$$

## 発電機の基本式

$$\dot{V}_0 = -\dot{Z}_0 \dot{I}_0 \quad \dots \textcircled{7}$$

$$\dot{V}_1 = \dot{E}_a - \dot{Z}_1 \dot{I}_1 \quad \dots \textcircled{8}$$

$$\dot{V}_2 = -\dot{Z}_2 \dot{I}_2 \quad \dots \textcircled{9}$$

## 電流/電圧の定義式・対称分式

$$\dot{V}_a = \dot{V}_0 + \dot{V}_1 + \dot{V}_2 \quad \dots \textcircled{11}$$

$$\dot{V}_b = \dot{V}_0 + a^2 \dot{V}_1 + a \dot{V}_2 \quad \dots \textcircled{3}$$

$$\dot{V}_c = \dot{V}_0 + a \dot{V}_1 + a^2 \dot{V}_2 \quad \dots \textcircled{4}$$

$$\dot{V}_0 = \frac{1}{3}(\dot{V}_a + \dot{V}_b + \dot{V}_c)$$

$$\dot{V}_1 = \frac{1}{3}(\dot{V}_a + a \dot{V}_b + a^2 \dot{V}_c)$$

$$\dot{V}_2 = \frac{1}{3}(\dot{V}_a + a^2 \dot{V}_b + a \dot{V}_c)$$

$$\dot{I}_a = \dot{I}_0 + \dot{I}_1 + \dot{I}_2 \quad \dots \textcircled{6}$$

$$\dot{I}_b = \dot{I}_0 + a^2 \dot{I}_1 + a \dot{I}_2 \quad \dots \textcircled{15}$$

$$\dot{I}_c = \dot{I}_0 + a \dot{I}_1 + a^2 \dot{I}_2 \quad \dots \textcircled{16}$$


$$\dot{I}_0 = \frac{1}{3}(\dot{I}_a + \dot{I}_b + \dot{I}_c)$$

$$\dot{I}_1 = \frac{1}{3}(\dot{I}_a + a \dot{I}_b + a^2 \dot{I}_c)$$

$$\dot{I}_2 = \frac{1}{3}(\dot{I}_a + a^2 \dot{I}_b + a \dot{I}_c)$$

## 対称座標法（2）《無負荷発電機の地絡計算4》

### 3線完全地絡

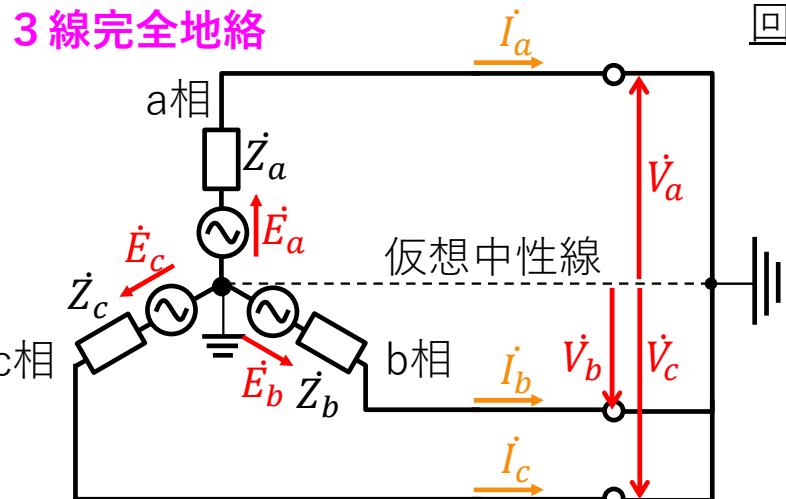

回路条件  $\dot{V}_a = \dot{V}_b = \dot{V}_c = 0 \cdots ①$

$$①, ③, ④, ⑤ \text{より } \dot{V}_0 = \dot{V}_1 = \dot{V}_2 = 0 \cdots ⑥$$

$$⑥, ⑦ \text{より } \dot{I}_0 = 0 \cdots ⑩$$

$$⑥, ⑧ \text{より } 0 = \dot{E}_a - \dot{Z}_1 \dot{I}_1 \quad \dot{I}_1 = \frac{\dot{E}_a}{\dot{Z}_1} \cdots ⑪$$

$$⑥, ⑨ \text{より } \dot{I}_2 = 0 \cdots ⑫$$

3線完全短絡と同じ

$$⑬ \text{に} ⑩, ⑪, ⑫ \text{を代入} \quad \dot{I}_a = \dot{I}_0 + \dot{I}_1 + \dot{I}_2 = 0 + \frac{\dot{E}_a}{\dot{Z}_1} + 0 = \frac{\dot{E}_a}{\dot{Z}_1}$$

$$⑭ \text{に} ⑩, ⑪, ⑫ \text{を代入} \quad \dot{I}_b = \dot{I}_0 + a^2 \dot{I}_1 + a \dot{I}_2 = 0 + \frac{a^2 \dot{E}_a}{\dot{Z}_1} + 0 = \frac{a^2 \dot{E}_a}{\dot{Z}_1}$$

$$⑮ \text{に} ⑩, ⑪, ⑫ \text{を代入} \quad \dot{I}_c = \dot{I}_0 + a \dot{I}_1 + a^2 \dot{I}_2 = 0 + \frac{a \dot{E}_a}{\dot{Z}_1} + 0 = \frac{a \dot{E}_a}{\dot{Z}_1}$$

### 発電機の基本式

$$\dot{V}_0 = -\dot{Z}_0 \dot{I}_0 \cdots ⑦$$

$$\dot{V}_1 = \dot{E}_a - \dot{Z}_1 \dot{I}_1 \cdots ⑧$$

$$\dot{V}_2 = -\dot{Z}_2 \dot{I}_2 \cdots ⑨$$

### 電流/電圧の定義式・対称分式

$$\dot{V}_a = \dot{V}_0 + \dot{V}_1 + \dot{V}_2$$

$$\dot{V}_b = \dot{V}_0 + a^2 \dot{V}_1 + a \dot{V}_2$$

$$\dot{V}_c = \dot{V}_0 + a \dot{V}_1 + a^2 \dot{V}_2$$

$$\dot{V}_0 = \frac{1}{3} (\dot{V}_a + \dot{V}_b + \dot{V}_c) \cdots ③$$

$$\dot{V}_1 = \frac{1}{3} (\dot{V}_a + a \dot{V}_b + a^2 \dot{V}_c) \cdots ④$$

$$\dot{V}_2 = \frac{1}{3} (\dot{V}_a + a^2 \dot{V}_b + a \dot{V}_c) \cdots ⑤$$

$$\dot{I}_a = \dot{I}_0 + \dot{I}_1 + \dot{I}_2 \cdots ⑬$$

$$\dot{I}_b = \dot{I}_0 + a^2 \dot{I}_1 + a \dot{I}_2 \cdots ⑭$$

$$\dot{I}_c = \dot{I}_0 + a \dot{I}_1 + a^2 \dot{I}_2 \cdots ⑮$$

$$\dot{I}_0 = \frac{1}{3} (\dot{I}_a + \dot{I}_b + \dot{I}_c)$$

$$\dot{I}_1 = \frac{1}{3} (\dot{I}_a + a \dot{I}_b + a^2 \dot{I}_c)$$

$$\dot{I}_2 = \frac{1}{3} (\dot{I}_a + a^2 \dot{I}_b + a \dot{I}_c)$$