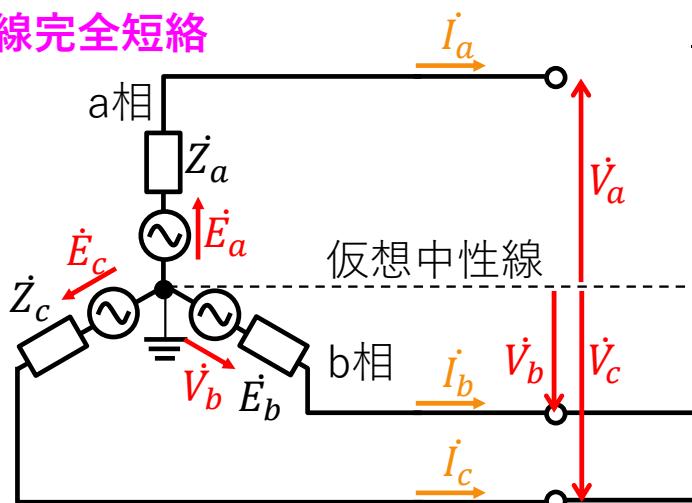


対称座標法（3）《無負荷発電機の短絡計算1》

2線完全短絡



回路条件

$$\dot{V}_b = \dot{V}_c \cdots ① \quad \dot{I}_a = 0 \cdots ② \quad \dot{I}_b + \dot{I}_c = 0 \cdots ③$$

③に④,⑤を代入 $2\dot{I}_0 = \dot{I}_1 + \dot{I}_2$

②,⑥より $\dot{I}_a = \dot{I}_0 + \dot{I}_1 + \dot{I}_2 = 3\dot{I}_0 = 0$

$$\therefore \dot{I}_0 = 0, \dot{I}_1 = -\dot{I}_2 \cdots ⑦$$

①に⑧,⑨を代入 $\dot{V}_1 = \dot{V}_2 \cdots ⑩$

⑩に⑦,⑪,⑫を代入 $\dot{I}_1 = \frac{\dot{E}_a}{\dot{Z}_1 + \dot{Z}_2} = -\dot{I}_2 \cdots ⑬$

④に⑦,⑬を代入

$$\dot{I}_b = \dot{I}_0 + a^2\dot{I}_1 + a\dot{I}_2 = \frac{a^2 - a}{\dot{Z}_1 + \dot{Z}_2} \dot{E}_a \cdots ⑭$$

③に⑭を代入 $\dot{I}_c = -\dot{I}_b = \frac{a - a^2}{\dot{Z}_1 + \dot{Z}_2} \dot{E}_a$

⑮に⑦を代入 $\dot{V}_0 = -\dot{Z}_0\dot{I}_0 = 0 \cdots ⑯$

⑪に⑬を代入 $\dot{V}_1 = \frac{\dot{Z}_2}{\dot{Z}_1 + \dot{Z}_2} \dot{E}_a = \dot{V}_2 \cdots ⑰$

⑲に⑯,⑰を代入 $\dot{V}_a = \frac{2\dot{Z}_2}{\dot{Z}_1 + \dot{Z}_2} \dot{E}_a$

⑧に⑯,⑰を代入 $\dot{V}_b = -\frac{\dot{Z}_2}{\dot{Z}_1 + \dot{Z}_2} \dot{E}_a = \dot{V}_c$

発電機の基本式

$$\dot{V}_0 = -\dot{Z}_0\dot{I}_0 \cdots ⑮$$

$$\dot{V}_1 = \dot{E}_a - \dot{Z}_1\dot{I}_1 \cdots ⑯$$

$$\dot{V}_2 = -\dot{Z}_2\dot{I}_2 \cdots ⑰$$

電流/電圧の定義式・対称分式

$$\dot{V}_a = \dot{V}_0 + \dot{V}_1 + \dot{V}_2 \cdots ⑱$$

$$\dot{V}_b = \dot{V}_0 + a^2\dot{V}_1 + a\dot{V}_2 \cdots ⑲$$

$$\dot{V}_c = \dot{V}_0 + a\dot{V}_1 + a^2\dot{V}_2 \cdots ⑳$$

$$\dot{V}_0 = \frac{1}{3}(\dot{V}_a + \dot{V}_b + \dot{V}_c)$$

$$\dot{V}_1 = \frac{1}{3}(\dot{V}_a + a\dot{V}_b + a^2\dot{V}_c)$$

$$\dot{V}_2 = \frac{1}{3}(\dot{V}_a + a^2\dot{V}_b + a\dot{V}_c)$$

$$\dot{I}_a = \dot{I}_0 + \dot{I}_1 + \dot{I}_2 \cdots ⑶$$

$$\dot{I}_b = \dot{I}_0 + a^2\dot{I}_1 + a\dot{I}_2 \cdots ⑷$$

$$\dot{I}_c = \dot{I}_0 + a\dot{I}_1 + a^2\dot{I}_2 \cdots ⑸$$

$$\dot{I}_0 = \frac{1}{3}(\dot{I}_a + \dot{I}_b + \dot{I}_c)$$

$$\dot{I}_1 = \frac{1}{3}(\dot{I}_a + a\dot{I}_b + a^2\dot{I}_c)$$

$$\dot{I}_2 = \frac{1}{3}(\dot{I}_a + a^2\dot{I}_b + a\dot{I}_c)$$

対称座標法 (3)

2線完全短絡の計算

$$\dot{V}_b = \dot{V}_c \cdots ① \quad \dot{I}_a = 0 \cdots ② \quad \dot{I}_b + \dot{I}_c = 0 \cdots ③$$

③に④,⑤を代入

$$\dot{I}_0 + a^2\dot{I}_1 + a\dot{I}_2 + (\dot{I}_0 + a\dot{I}_1 + a^2\dot{I}_2) = 0$$

$$2\dot{I}_0 + (a^2 + a)(\dot{I}_1 + \dot{I}_2) = 0$$

$$a^2 + a = -1 \text{ より } 2\dot{I}_0 = \dot{I}_1 + \dot{I}_2$$

$$②,⑥ \text{ より } \dot{I}_a = \dot{I}_0 + \dot{I}_1 + \dot{I}_2 = 3\dot{I}_0 = 0$$

$$\therefore \dot{I}_0 = 0, \dot{I}_1 = -\dot{I}_2 \cdots ⑦$$

①より $\dot{V}_b - \dot{V}_c = 0$ に⑧,⑨を代入

$$\dot{V}_0 + a^2\dot{V}_1 + a\dot{V}_2 - (\dot{V}_0 + a\dot{V}_1 + a^2\dot{V}_2) = 0$$

$$(a^2 - a)(\dot{V}_1 - \dot{V}_2) = 0$$

$$a^2 - a \neq 0 \text{ より } \dot{V}_1 = \dot{V}_2 \cdots ⑩$$

⑩に⑪,⑫,⑦を代入

$$\dot{E}_a - \dot{Z}_1\dot{I}_1 = -\dot{Z}_2\dot{I}_2 = \dot{Z}_2\dot{I}_1$$

$$\dot{I}_1 = \frac{\dot{E}_a}{\dot{Z}_1 + \dot{Z}_2} = -\dot{I}_2 \cdots ⑬$$

④に⑦,⑬を代入

$$\dot{I}_b = \dot{I}_0 + a^2\dot{I}_1 + a\dot{I}_2 = \frac{a^2 - a}{\dot{Z}_1 + \dot{Z}_2} \dot{E}_a \cdots ⑭$$

$$③ \text{ に } ⑭ \text{ を代入 } \dot{I}_c = -\dot{I}_b = \frac{a - a^2}{\dot{Z}_1 + \dot{Z}_2} \dot{E}_a$$

$$⑮ \text{ に } ⑦ \text{ を代入 } \dot{V}_0 = -\dot{Z}_0\dot{I}_0 = 0 \cdots ⑯$$

⑪に⑬を代入

$$\dot{V}_1 = \dot{E}_a - \frac{\dot{Z}_1\dot{E}_a}{\dot{Z}_1 + \dot{Z}_2} = \frac{\dot{Z}_2}{\dot{Z}_1 + \dot{Z}_2} \dot{E}_a = \dot{V}_2 \cdots ⑰$$

⑯に⑯,⑰を代入

$$\dot{V}_a = 0 + \frac{\dot{Z}_2}{\dot{Z}_1 + \dot{Z}_2} \dot{E}_a + \frac{\dot{Z}_2}{\dot{Z}_1 + \dot{Z}_2} \dot{E}_a = \frac{2\dot{Z}_2}{\dot{Z}_1 + \dot{Z}_2} \dot{E}_a$$

⑧に⑯,⑰を代入

$$\begin{aligned} \dot{V}_b &= 0 + \frac{a^2\dot{Z}_2}{\dot{Z}_1 + \dot{Z}_2} \dot{E}_a + \frac{a\dot{Z}_2}{\dot{Z}_1 + \dot{Z}_2} \dot{E}_a = \frac{(a^2 + a)\dot{Z}_2}{\dot{Z}_1 + \dot{Z}_2} \dot{E}_a \\ &= -\frac{\dot{Z}_2}{\dot{Z}_1 + \dot{Z}_2} \dot{E}_a = \dot{V}_c \end{aligned}$$

発電機の基本式

$$\dot{V}_0 = -\dot{Z}_0\dot{I}_0 \cdots ⑮$$

$$\dot{V}_1 = \dot{E}_a - \dot{Z}_1\dot{I}_1 \cdots ⑯$$

$$\dot{V}_2 = -\dot{Z}_2\dot{I}_2 \cdots ⑰$$

電流/電圧の定義式・対称分式

$$\dot{V}_a = \dot{V}_0 + \dot{V}_1 + \dot{V}_2 \cdots ⑱$$

$$\dot{V}_b = \dot{V}_0 + a^2\dot{V}_1 + a\dot{V}_2 \cdots ⑲$$

$$\dot{V}_c = \dot{V}_0 + a\dot{V}_1 + a^2\dot{V}_2 \cdots ⑳$$

$$\dot{V}_0 = \frac{1}{3}(\dot{V}_a + \dot{V}_b + \dot{V}_c)$$

$$\dot{V}_1 = \frac{1}{3}(\dot{V}_a + a\dot{V}_b + a^2\dot{V}_c)$$

$$\dot{V}_2 = \frac{1}{3}(\dot{V}_a + a^2\dot{V}_b + a\dot{V}_c)$$

$$\dot{I}_a = \dot{I}_0 + \dot{I}_1 + \dot{I}_2 \cdots ⑶$$

$$\dot{I}_b = \dot{I}_0 + a^2\dot{I}_1 + a\dot{I}_2 \cdots ⑷$$

$$\dot{I}_c = \dot{I}_0 + a\dot{I}_1 + a^2\dot{I}_2 \cdots ⑸$$


$$\dot{I}_0 = \frac{1}{3}(\dot{I}_a + \dot{I}_b + \dot{I}_c)$$

$$\dot{I}_1 = \frac{1}{3}(\dot{I}_a + a\dot{I}_b + a^2\dot{I}_c)$$

$$\dot{I}_2 = \frac{1}{3}(\dot{I}_a + a^2\dot{I}_b + a\dot{I}_c)$$

対称座標法（3）《無負荷発電機の短絡計算2》

2線不完全短絡

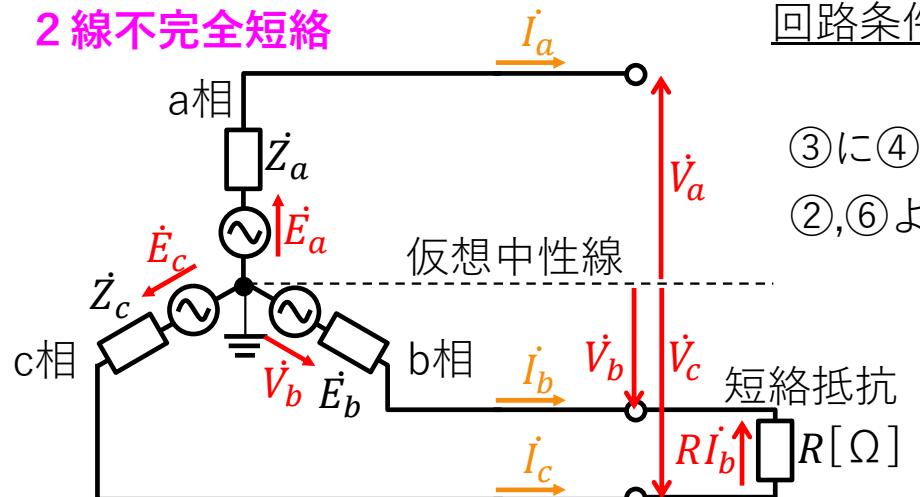

④に⑦, ⑬を代入

$$I_b = \frac{a^2 - a}{Z_1 + Z_2 + R} E_a \quad \dots ⑭$$

⑯に⑦を代入

$$\dot{V}_0 = -\dot{Z}_0 I_0 = 0 \quad \dots ⑯$$

⑰に⑯, ⑰, ⑱を代入

$$\dot{V}_a = \frac{2\dot{Z}_2 + R}{\dot{Z}_1 + \dot{Z}_2 + R} E_a$$

$$\text{回路条件 } \dot{V}_b - \dot{V}_c = R \dot{I}_b \quad \dots ①$$

$$\dot{I}_a = 0 \quad \dots ② \quad \dot{I}_b + \dot{I}_c = 0 \quad \dots ③$$

$$\text{③に④, ⑤を代入 } 2\dot{I}_0 = \dot{I}_1 + \dot{I}_2$$

$$\text{②, ⑥より } \dot{I}_a = \dot{I}_0 + \dot{I}_1 + \dot{I}_2 = 3\dot{I}_0 = 0$$

$$\therefore \dot{I}_0 = 0, \dot{I}_1 = -\dot{I}_2 \quad \dots ⑦$$

①に④, ⑦, ⑧, ⑨を代入

$$\dot{V}_1 - \dot{V}_2 = R \dot{I}_1 \quad \dots ⑩$$

⑩に⑪, ⑫, ⑦を代入

$$\dot{I}_1 = \frac{\dot{E}_a}{\dot{Z}_1 + \dot{Z}_2 + R} = -\dot{I}_2 \quad \dots ⑬$$

③に⑭を代入

$$\dot{I}_c = -\dot{I}_b = \frac{a - a^2}{\dot{Z}_1 + \dot{Z}_2 + R} E_a$$

⑪に⑬を代入

$$\dot{V}_1 = \frac{\dot{Z}_2 + R}{\dot{Z}_1 + \dot{Z}_2 + R} E_a \quad \dots ⑯$$

⑧に⑯, ⑰, ⑱を代入

$$\dot{V}_b = \frac{-\dot{Z}_2 + a^2 R}{\dot{Z}_1 + \dot{Z}_2 + R} E_a$$

⑫に⑬を代入

$$\dot{V}_2 = \frac{\dot{Z}_2}{\dot{Z}_1 + \dot{Z}_2 + R} E_a \quad \dots ⑯$$

⑨に⑯, ⑰, ⑱を代入

$$\dot{V}_c = \frac{-\dot{Z}_2 + aR}{\dot{Z}_1 + \dot{Z}_2 + R} E_a$$

発電機の基本式

$$\dot{V}_0 = -\dot{Z}_0 \dot{I}_0 \quad \dots ⑮$$

$$\dot{V}_1 = \dot{E}_a - \dot{Z}_1 \dot{I}_1 \quad \dots ⑯$$

$$\dot{V}_2 = -\dot{Z}_2 \dot{I}_2 \quad \dots ⑰$$

電流/電圧の定義式・対称分式

$$\dot{V}_a = \dot{V}_0 + \dot{V}_1 + \dot{V}_2 \quad \dots ⑲$$

$$\dot{V}_b = \dot{V}_0 + a^2 \dot{V}_1 + a \dot{V}_2 \quad \dots ⑳$$

$$\dot{V}_c = \dot{V}_0 + a \dot{V}_1 + a^2 \dot{V}_2 \quad \dots ㉑$$

$$\dot{V}_0 = \frac{1}{3} (\dot{V}_a + \dot{V}_b + \dot{V}_c)$$

$$\dot{V}_1 = \frac{1}{3} (\dot{V}_a + a \dot{V}_b + a^2 \dot{V}_c)$$

$$\dot{V}_2 = \frac{1}{3} (\dot{V}_a + a^2 \dot{V}_b + a \dot{V}_c)$$

$$\dot{I}_a = \dot{I}_0 + \dot{I}_1 + \dot{I}_2 \quad \dots ㉒$$

$$\dot{I}_b = \dot{I}_0 + a^2 \dot{I}_1 + a \dot{I}_2 \quad \dots ㉓$$

$$\dot{I}_c = \dot{I}_0 + a \dot{I}_1 + a^2 \dot{I}_2 \quad \dots ㉔$$

$$\dot{I}_0 = \frac{1}{3} (\dot{I}_a + \dot{I}_b + \dot{I}_c)$$

$$\dot{I}_1 = \frac{1}{3} (\dot{I}_a + a \dot{I}_b + a^2 \dot{I}_c)$$

$$\dot{I}_2 = \frac{1}{3} (\dot{I}_a + a^2 \dot{I}_b + a \dot{I}_c)$$

対称座標法（2） 2線不完全短絡の計算

$$\dot{V}_b - \dot{V}_c = R\dot{I}_b \quad \dots \textcircled{1}$$

$$\dot{I}_a = 0 \quad \dots \textcircled{2}$$

$$\dot{I}_b + \dot{I}_c = 0 \quad \dots \textcircled{3}$$

③に④,⑤を代入

$$\dot{I}_0 + a^2\dot{I}_1 + a\dot{I}_2 + (\dot{I}_0 + a\dot{I}_1 + a^2\dot{I}_2) = 0$$

$$2\dot{I}_0 + (a^2 + a)(\dot{I}_1 + \dot{I}_2) = 0$$

$$a^2 + a = -1 \text{ より } 2\dot{I}_0 = \dot{I}_1 + \dot{I}_2$$

$$\textcircled{2}, \textcircled{6} \text{ より } \dot{I}_a = \dot{I}_0 + \dot{I}_1 + \dot{I}_2 = 3\dot{I}_0 = 0$$

$$\therefore \dot{I}_0 = 0, \dot{I}_1 = -\dot{I}_2 \quad \dots \textcircled{7}$$

①より $\dot{V}_b - \dot{V}_c = R\dot{I}_b$ に④,⑦,⑧,⑨を代入

$$\dot{V}_0 + a^2\dot{V}_1 + a\dot{V}_2 - (\dot{V}_0 + a\dot{V}_1 + a^2\dot{V}_2) = R\dot{I}_b$$

$$(a^2 - a)(\dot{V}_1 - \dot{V}_2) = R(\dot{I}_0 + a^2\dot{I}_1 + a\dot{I}_2)$$

$$(a^2 - a)(\dot{V}_1 - \dot{V}_2) = R(a^2 - a)\dot{I}_1$$

$$\dot{V}_1 - \dot{V}_2 = R\dot{I}_1 \quad \dots \textcircled{10}$$

⑩に⑪,⑫,⑦を代入

$$\dot{E}_a - \dot{Z}_1\dot{I}_1 - \dot{Z}_2\dot{I}_2 = \dot{E}_a - (\dot{Z}_1 + \dot{Z}_2)\dot{I}_1 = R\dot{I}_1$$

$$\dot{I}_1 = \frac{\dot{E}_a}{\dot{Z}_1 + \dot{Z}_2 + R} = -\dot{I}_2 \quad \dots \textcircled{13}$$

④に⑦,⑬を代入

$$\dot{I}_b = \dot{I}_0 + a^2\dot{I}_1 + a\dot{I}_2 = \frac{a^2 - a}{\dot{Z}_1 + \dot{Z}_2 + R} \dot{E}_a \quad \dots \textcircled{14}$$

$$\textcircled{3} \text{ に } \textcircled{14} \text{ を代入 } \dot{I}_c = -\dot{I}_b = \frac{a - a^2}{\dot{Z}_1 + \dot{Z}_2 + R} \dot{E}_a$$

$$\textcircled{15} \text{ に } \textcircled{7} \text{ を代入 } \dot{V}_0 = -\dot{Z}_0\dot{I}_0 = 0 \quad \dots \textcircled{16}$$

⑪に⑬を代入

$$\dot{V}_1 = \dot{E}_a - \frac{\dot{Z}_1\dot{E}_a}{\dot{Z}_1 + \dot{Z}_2 + R} = \frac{\dot{Z}_2 + R}{\dot{Z}_1 + \dot{Z}_2 + R} \dot{E}_a \quad \dots \textcircled{17}$$

$$\textcircled{12} \text{ に } \textcircled{13} \text{ を代入 } \dot{V}_2 = \frac{\dot{Z}_2}{\dot{Z}_1 + \dot{Z}_2 + R} \dot{E}_a \quad \dots \textcircled{18}$$

⑯に⑯,⑰,⑱を代入

$$\dot{V}_a = \frac{\dot{Z}_2 + R}{\dot{Z}_1 + \dot{Z}_2 + R} \dot{E}_a + \frac{\dot{Z}_2}{\dot{Z}_1 + \dot{Z}_2 + R} \dot{E}_a = \frac{2\dot{Z}_2 + R}{\dot{Z}_1 + \dot{Z}_2 + R} \dot{E}_a$$

⑮に⑯,⑰,⑱を代入

$$\begin{aligned} \dot{V}_b &= \frac{a^2(\dot{Z}_2 + R)}{\dot{Z}_1 + \dot{Z}_2 + R} \dot{E}_a + \frac{a\dot{Z}_2}{\dot{Z}_1 + \dot{Z}_2 + R} \dot{E}_a \\ &= \frac{(a^2 + a)\dot{Z}_2 + a^2R}{\dot{Z}_1 + \dot{Z}_2 + R} \dot{E}_a = \frac{-\dot{Z}_2 + a^2R}{\dot{Z}_1 + \dot{Z}_2 + R} \dot{E}_a \end{aligned}$$

⑯に⑯,⑰,⑱を代入

$$\dot{V}_c = \frac{a(\dot{Z}_2 + R)}{\dot{Z}_1 + \dot{Z}_2 + R} \dot{E}_a + \frac{a^2\dot{Z}_2}{\dot{Z}_1 + \dot{Z}_2 + R} \dot{E}_a = \frac{-\dot{Z}_2 + aR}{\dot{Z}_1 + \dot{Z}_2 + R} \dot{E}_a$$

発電機の基本式

$$\dot{V}_0 = -\dot{Z}_0\dot{I}_0 \quad \dots \textcircled{15}$$

$$\dot{V}_1 = \dot{E}_a - \dot{Z}_1\dot{I}_1 \quad \dots \textcircled{11}$$

$$\dot{V}_2 = -\dot{Z}_2\dot{I}_2 \quad \dots \textcircled{12}$$

電流/電圧の定義式・対称分式

$$\dot{V}_a = \dot{V}_0 + \dot{V}_1 + \dot{V}_2 \quad \dots \textcircled{19}$$

$$\dot{V}_b = \dot{V}_0 + a^2\dot{V}_1 + a\dot{V}_2 \quad \dots \textcircled{8}$$

$$\dot{V}_c = \dot{V}_0 + a\dot{V}_1 + a^2\dot{V}_2 \quad \dots \textcircled{9}$$

$$\dot{V}_0 = \frac{1}{3}(\dot{V}_a + \dot{V}_b + \dot{V}_c)$$

$$\dot{V}_1 = \frac{1}{3}(\dot{V}_a + a\dot{V}_b + a^2\dot{V}_c)$$

$$\dot{V}_2 = \frac{1}{3}(\dot{V}_a + a^2\dot{V}_b + a\dot{V}_c)$$

$$\dot{I}_a = \dot{I}_0 + \dot{I}_1 + \dot{I}_2 \quad \dots \textcircled{6}$$

$$\dot{I}_b = \dot{I}_0 + a^2\dot{I}_1 + a\dot{I}_2 \quad \dots \textcircled{4}$$

$$\dot{I}_c = \dot{I}_0 + a\dot{I}_1 + a^2\dot{I}_2 \quad \dots \textcircled{5}$$


$$\dot{I}_0 = \frac{1}{3}(\dot{I}_a + \dot{I}_b + \dot{I}_c)$$

$$\dot{I}_1 = \frac{1}{3}(\dot{I}_a + a\dot{I}_b + a^2\dot{I}_c)$$

$$\dot{I}_2 = \frac{1}{3}(\dot{I}_a + a^2\dot{I}_b + a\dot{I}_c)$$

対称座標法（3）《無負荷発電機の短絡計算3》

3線完全短絡

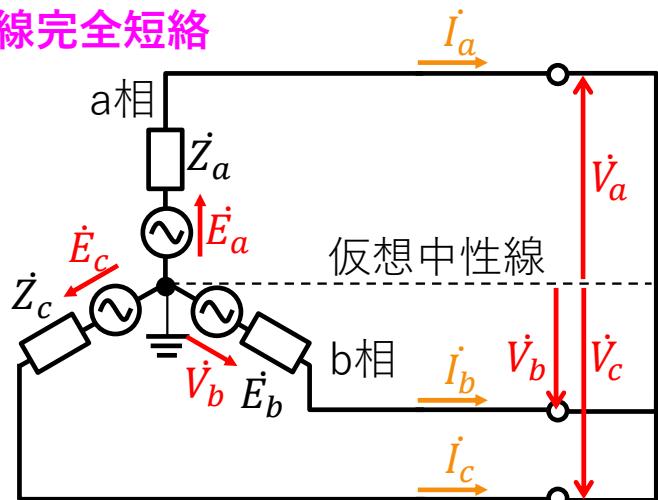

回路条件 $\dot{I}_a + \dot{I}_b + \dot{I}_c = 0 \quad \cdots ①$

$$\dot{V}_a = \dot{V}_b = \dot{V}_c \quad \cdots ②$$

$$①, ③ \text{より } \dot{I}_0 = \frac{1}{3}(\dot{I}_a + \dot{I}_b + \dot{I}_c) = 0 \quad \cdots ④$$

$$④, ⑤ \text{より } \dot{V}_0 = -\dot{Z}_0 \dot{I}_0 = 0 \quad \cdots ⑥$$

$$②, ⑦ \text{より } \dot{V}_1 = \frac{1}{3}(1 + a + a^2)\dot{V}_a = 0 \quad \cdots ⑨$$

$$②, ⑧ \text{より } \dot{V}_2 = \frac{1}{3}(1 + a^2 + a)\dot{V}_a = 0 \quad \cdots ⑩$$

$$⑥, ⑨, ⑩ \text{より } \dot{V}_0 = \dot{V}_1 = \dot{V}_2 = 0 \quad \cdots ⑪$$

$$⑪, ⑫, ⑬, ⑭ \text{より } \dot{V}_a = \dot{V}_b = \dot{V}_c = 0$$

3線完全地絡と同じ回路条件

$$\therefore \dot{I}_a = \frac{\dot{E}_a}{\dot{Z}_1} \quad \dot{I}_b = \frac{a^2 \dot{E}_a}{\dot{Z}_1} \quad \dot{I}_c = \frac{a \dot{E}_a}{\dot{Z}_1}$$

$\dot{Z}_1 = \dot{Z}_2 = \dot{Z}$ のとき、3線完全短絡電流 \dot{I}_{s3} と 2線完全短絡電流 \dot{I}_{s2} の大きさは

$$|\dot{I}_{s3}| = \left| \frac{\dot{E}_a}{\dot{Z}} \right| = \frac{E}{Z} \quad |\dot{I}_{s2}| = \left| \frac{a^2 - a}{2\dot{Z}} \dot{E}_a \right| = \left| \frac{j\sqrt{3}}{2\dot{Z}} \dot{E}_a \right| = \frac{\sqrt{3}}{2} \cdot \frac{E}{Z} \quad |\dot{I}_{s2}| = \frac{\sqrt{3}}{2} |\dot{I}_{s3}| \doteq 0.87 |\dot{I}_{s3}|$$

発電機の基本式

$$\dot{V}_0 = -\dot{Z}_0 \dot{I}_0 \quad \cdots ⑤$$

$$\dot{V}_1 = \dot{E}_a - \dot{Z}_1 \dot{I}_1$$

$$\dot{V}_2 = -\dot{Z}_2 \dot{I}_2$$

電流/電圧の定義式・対称分式

$$\dot{V}_a = \dot{V}_0 + \dot{V}_1 + \dot{V}_2 \quad \cdots ⑫$$

$$\dot{V}_b = \dot{V}_0 + a^2 \dot{V}_1 + a \dot{V}_2 \quad \cdots ⑬$$

$$\dot{V}_c = \dot{V}_0 + a \dot{V}_1 + a^2 \dot{V}_2 \quad \cdots ⑭$$

$$\dot{V}_0 = \frac{1}{3}(\dot{V}_a + \dot{V}_b + \dot{V}_c)$$

$$\dot{V}_1 = \frac{1}{3}(\dot{V}_a + a\dot{V}_b + a^2\dot{V}_c) \quad \cdots ⑦$$

$$\dot{V}_2 = \frac{1}{3}(\dot{V}_a + a^2\dot{V}_b + a\dot{V}_c) \quad \cdots ⑧$$

$$\dot{I}_a = \dot{I}_0 + \dot{I}_1 + \dot{I}_2$$

$$\dot{I}_b = \dot{I}_0 + a^2 \dot{I}_1 + a \dot{I}_2$$

$$\dot{I}_c = \dot{I}_0 + a \dot{I}_1 + a^2 \dot{I}_2$$

$$\dot{I}_0 = \frac{1}{3}(\dot{I}_a + \dot{I}_b + \dot{I}_c) \quad \cdots ③$$

$$\dot{I}_1 = \frac{1}{3}(\dot{I}_a + a\dot{I}_b + a^2\dot{I}_c)$$

$$\dot{I}_2 = \frac{1}{3}(\dot{I}_a + a^2\dot{I}_b + a\dot{I}_c)$$