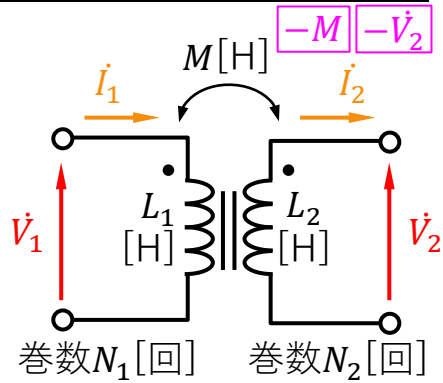


相互インダクタンス (11)



巻数比 : $a = \frac{N_1}{N_2}$

$$\begin{cases} \dot{V}_1 = j\omega L_1 \dot{I}_1 - j\omega M \dot{I}_2 \\ \dot{V}_2 = -j\omega L_2 \dot{I}_2 + j\omega M \dot{I}_1 \end{cases}$$

【理想変成器の条件】

- ・漏れ磁束ゼロ (結合係数 $k = 1$)
- ・エネルギー損失なし
 - 巻線抵抗ゼロ
 - 鉄心の透磁率 ∞ → $L_1, L_2 = \infty$ (巻数比は保つ)

《理想変成器》

磁気抵抗 : R_m [A/Wb]

$$L_1 = \frac{N_1^2}{R_m} \quad L_2 = \frac{N_2^2}{R_m} \quad M = k\sqrt{L_1 L_2} = \sqrt{\frac{N_1^2}{R_m} \cdot \frac{N_2^2}{R_m}} = \frac{N_1 N_2}{R_m} \quad \therefore R_m = \frac{N_1 N_2}{M}$$

$$L_1 = \frac{N_1^2}{R_m} = \frac{N_1^2}{\frac{N_1 N_2}{M}} = \frac{N_1 M}{N_2} = aM \quad L_2 = \frac{N_2^2}{R_m} = \frac{N_2^2}{\frac{N_1 N_2}{M}} = \frac{N_2 M}{N_1} = \frac{M}{a} \quad \therefore \begin{cases} L_1 = aM \\ L_2 = \frac{M}{a} \end{cases}$$

$$\frac{\dot{V}_1}{\dot{V}_2} = \frac{j\omega L_1 \dot{I}_1 - j\omega M \dot{I}_2}{-j\omega L_2 \dot{I}_2 + j\omega M \dot{I}_1} = \frac{L_1 \dot{I}_1 - M \dot{I}_2}{-L_2 \dot{I}_2 + M \dot{I}_1} = \frac{aM \dot{I}_1 - M \dot{I}_2}{-\frac{M}{a} \dot{I}_2 + M \dot{I}_1} = \frac{a \left(M \dot{I}_1 - \frac{M}{a} \dot{I}_2 \right)}{M \dot{I}_1 - \frac{M}{a} \dot{I}_2} = a = \frac{N_1}{N_2}$$

$$\dot{I}_1 = \frac{\dot{V}_1 + j\omega M \dot{I}_2}{j\omega L_1} = \frac{\dot{V}_1}{j\omega L_1} + \frac{M \dot{I}_2}{aM} = \frac{\dot{V}_1}{j\omega L_1} + \frac{M \dot{I}_2}{L_1} = \frac{\dot{V}_1}{j\omega L_1} + \frac{\dot{I}_2}{a}$$

$$L_1 \rightarrow \infty \text{ より、 } \dot{I}_1 = 0 + \frac{\dot{I}_2}{a} = \frac{\dot{I}_2}{a} \quad \frac{\dot{I}_1}{\dot{I}_2} = \frac{1}{a} = \frac{N_2}{N_1}$$

$$\begin{aligned} \dot{V}_1 : \dot{V}_2 &= N_1 : N_2 \\ \dot{I}_1 : \dot{I}_2 &= N_2 : N_1 \end{aligned}$$

$$\frac{|\dot{V}_1| \cdot |\dot{I}_1|}{|\dot{V}_2| \cdot |\dot{I}_2|} = a \cdot \frac{1}{a} = 1$$

理想変成器は完全な電力変換器